
Contents

Preface v

Chapter 1 Introduction

- 1-1 What is electronics? 1
- 1-2 Applications of electronics in biology 1

Chapter 2 Elementary principles of electronics

- 2-1 Introduction 3
- 2-2 The nature of electric current 3
- 2-3 Charge, current, voltage, resistance, and power 6
- 2-4 Direct and alternating currents 6
- 2-5 Capacitance 7
- 2-6 Electric field 9
- 2-7 Shielding 9
- 2-8 Magnetism 10
- 2-9 Motor effect 10
- 2-10 Generator effect 11
- 2-11 Reactance, resistance, and impedance 11
- 2-12 Transformers 13
- 2-13 Time constants 13
- 2-14 Resonant circuits 15
- 2-15 Applications 15
- 2-16 Passive and active circuits 18
- 2-17 Vacuum tubes 19
- 2-18 Thermionic emission 20
- 2-19 Types of cathodes 20
- 2-20 Screen-grid tubes 20
- 2-21 Diodes 21
- 2-22 Transistors 22
- 2-23 Resistive loading effects 22
- 2-24 Equivalent signal sources and Thévenin's theorem 23
- 2-25 Effects of reactive loading 24

Chapter 3 Simple vacuum-tube circuits

3-1	Basic vacuum-tube circuits	26
3-2	Capacitor coupling	28
3-3	Multistage amplifiers	29
3-4	A practical amplifier	30
3-5	Push-pull amplifiers	31
3-6	Differential versus single-ended amplifiers	32

Chapter 4 Oscillographs

4-1	Oscillographs	34
4-2	The cathode-ray oscillograph	34
4-3	Mechanical oscillographs	36
4-4	Direct-writing oscillographs	36
4-5	Moving-coil recorders	36
4-6	Moving-iron recorders	38
4-7	Crystal recorders	39
4-8	Ink jet recorders	40
4-9	Servo recorders	40
4-10	Recording media for direct-writing oscillographs	41
4-11	Optical oscillographs	41

Chapter 5 Electrophysiological electronic practice

5-1	The electrophysiological amplifier	43
5-2	Sensitivity	43
5-3	Noise	44
5-4	Frequency response	45
5-5	Need for differential amplifiers	47
5-6	A practical amplifier	48
5-7	A preamplifier	50
5-8	Cathode-ray connections	51
5-9	Shielding	51
5-10	Calibration	52
5-11	Operating the amplifier	52
5-12	Interpretation of pattern	53
5-13	Gain controls	55
5-14	Use with cathode-ray amplifier	55
5-15	Use as preamplifier	56
5-16	Amplifier noise	56
5-17	Power-line pickup	57

Chapter 6 Semiconductor electronics

6-1	The importance of semiconductors	59
6-2	Thermistors	59

6-3	Photoresistors	60
6-4	Effect of impurities	60
6-5	Semiconductor diodes	61
6-6	Transistors	63
6-7	<i>pnp</i> and <i>npn</i> transistors	64
6-8	Other transistor types	64

Chapter 7 Transistor circuits

7-1	Transistors compared with vacuum tubes	65
7-2	Transistor characteristics	65
7-3	<i>npn</i> and <i>pnp</i> transistors	70
7-4	Silicon and germanium transistors	70
7-5	Basic transistor circuits	70
7-6	Phase relations	72
7-7	Selection of operating conditions	72
7-8	Multistage transistor amplifiers	73
7-9	Complementary coupling	77
7-10	Output phase	77

Chapter 8 Feedback

8-1	What is feedback?	78
8-2	Negative feedback	78
8-3	Intuitive explanation	79
8-4	Mathematical interpretation	81
8-5	Effect on impedance	82

Chapter 9 Differential amplifiers

9-1	What a differential amplifier is and does	84
9-2	Mathematical expression of performance	85
9-3	Types of differential amplifiers	86
9-4	Limitations of differential amplifiers	91

Chapter 10 Amplifier types and designs

10-1	Types of amplifiers	93
10-2	Transistors versus vacuum tubes	93
10-3	Bioelectric amplifier design	95
10-4	The chopper amplifier	97
10-5	Advantages of chopper amplifiers	99
10-6	Limitations of chopper amplifiers	100
10-7	Types of chopper amplifiers	101
10-8	Demodulator circuits	102

10-9	Types of choppers	104
10-10	Diode chopper	105
10-11	Transistor chopper	105
10-12	Photoelectric choppers	106

Chapter 11 Power supplies

11-1	Need for power supplies	107
11-2	Types of supplies	107
11-3	Batteries	107
11-4	Power-line operated supplies	109
11-5	Rectifier circuits	111
11-6	Types of rectifiers	115
11-7	Filters	115
11-8	Regulated supplies	116
11-9	Regulating transformers	121

Chapter 12 Transducers

12-1	What a transducer is	123
12-2	Mechanical-electrical transducers	123
12-3	Strain gages	124
12-4	Strain-gage transducers	126
12-5	Balancing the bridge	127
12-6	Calibrating the bridge	128
12-7	Carrier-current method	128
12-8	Variable-inductance transducers	130
12-9	Differential-transformer transducers	131
12-10	Piezoelectric transducers	133
12-11	Capacitance transducers	134
12-12	Photoelectric transducers	134
12-13	Temperature transducers	135
12-14	Thermocouples	135
12-15	Resistance thermometers	137
12-16	<i>pn</i> -junction temperature transducer	139

Chapter 13 Electrodes

13-1	Types of electrodes	141
13-2	Polarizable electrodes	141
13-3	Non-polarizable electrodes	143
13-4	Making an Ag-AgCl electrode	144
13-5	Use of Ag-AgCl electrodes	144
13-6	Salt-bridge or fluid electrodes	145
13-7	Metal microelectrodes	146

Chapter 14 High impedance amplifiers

14-1	Characteristics of high input-impedance amplifiers	148
14-2	Electrometer input vacuum tubes	149
14-3	Sources of input capacitance	153
14-4	Reducing the effects of input capacitance	154
14-5	Limitations of compensation techniques	157
14-6	Cathode-follower inputs	158
14-7	Field-effect transistors	159

Chapter 15 Stimulators

15-1	Use of stimulators	161
15-2	Selection of current forms	161
15-3	Constant voltage versus constant current stimulation	162
15-4	Effect of d-c component	163
15-5	Stimulus artifacts	164
15-6	Sources of stimulus artifacts	165
15-7	Elimination of stimulus artifacts	168

Chapter 16 Frequency and transient response

16-1	Amplitude and phase response	169
16-2	Linear delay and delay error	172
16-3	Transient response	173
16-4	Square-wave and sine-wave responses	174
16-5	Frequency analysis of transients	176
16-6	Application to oscillograph performance	176

Index 181